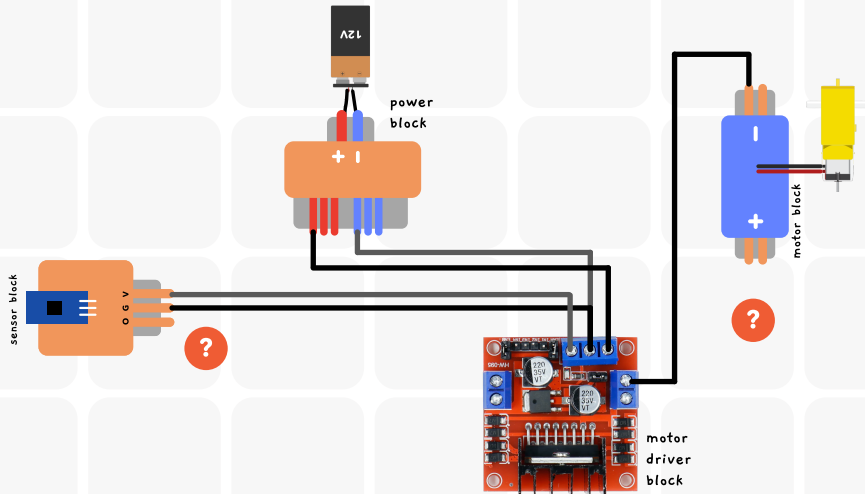



circuit 1: ir sensor + motor block

Task: Use a motor driver to control a motor block. Control the direction of the motor by changing Out PIN of the sensor block. Can you complete the missing wire **?** in the circuit and change the direction of the motor using the sensor?



circuit 2: dual ir sensor circuit

Task: Use a motor driver to control 2 motor blocks. The signal to the motor block (A) is sent through the IR sensor block(A) and the signal to the motor block (B) is sent through the IR sensor block(B). Can you complete the missing wire **?** in the circuit and control the motors using the sensors?

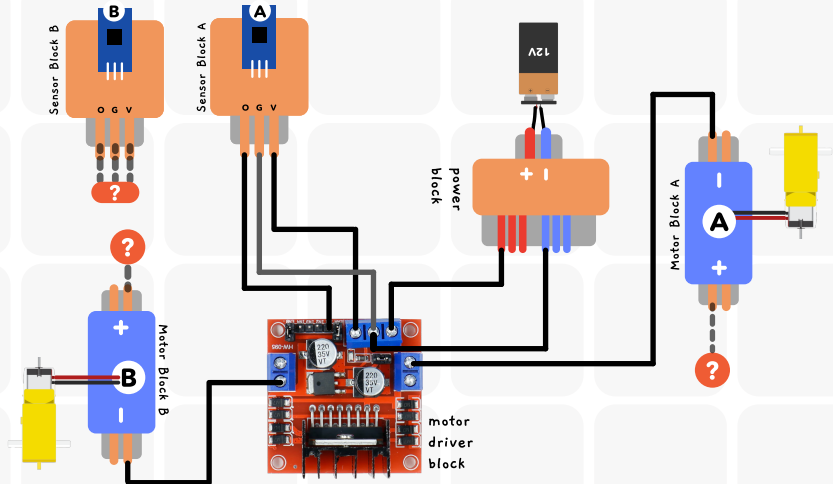


circuit 3: dual motor blocks + ir sensors

Task: Use a motor driver to control 2 motor blocks.

Motor block (A) must turn Right and Motor block (b) must turn left.

Use the Sensor OUT pins to control the direction of the motors and complete the missing wires **?** in the circuit.

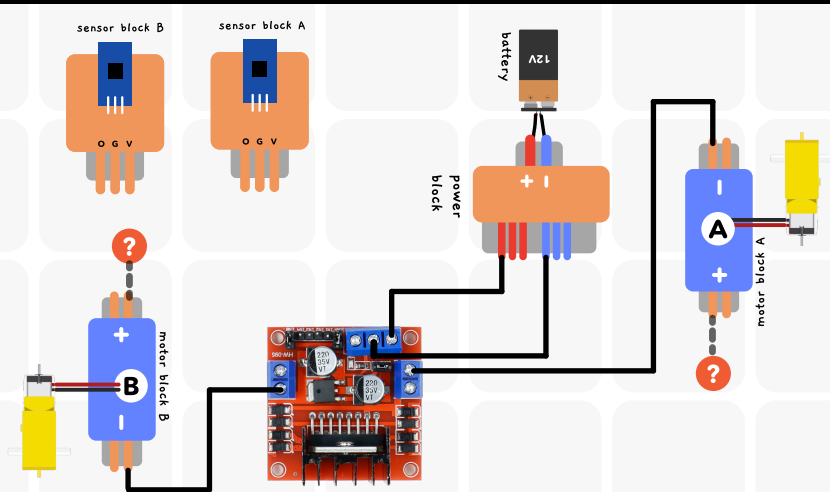

circuit 4: ir sensor + motor block

Task: Send a signal to the motor driver block using an IR sensor block. Adjust the range of the IR Sensor to detect objects that are close enough. Complete the missing wires **?** in the circuit.

