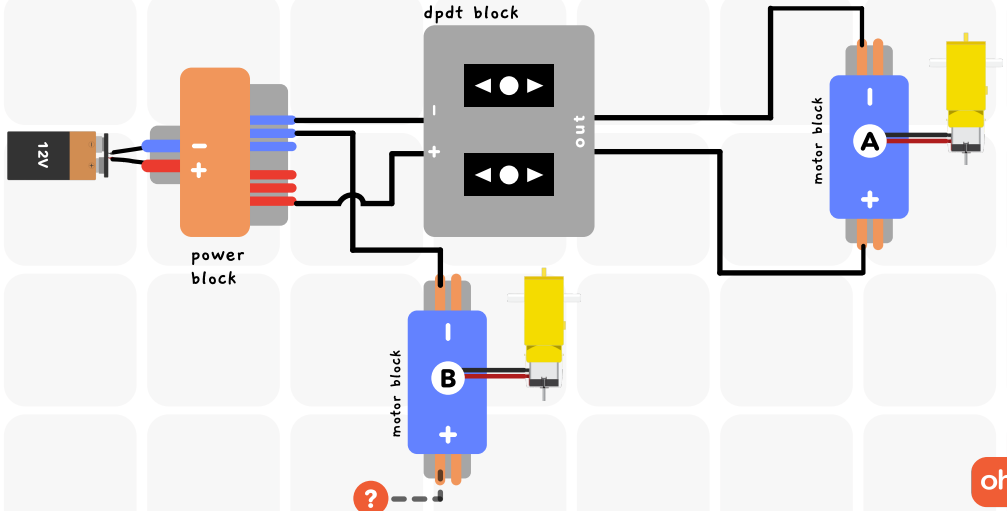



circuit 1: dpdt block + motor block

Task: Control motor block (A) using a dpdt block while motor block (B) remain should remain ON. Can you complete the missing wire ? in the circuit?




circuit 2: potentiometer + dual motor blocks

Task: A circuit uses a pot block to control the speed of 2 motor blocks connected in series. Can you complete missing wire **?** in the circuit and adjust the speed?

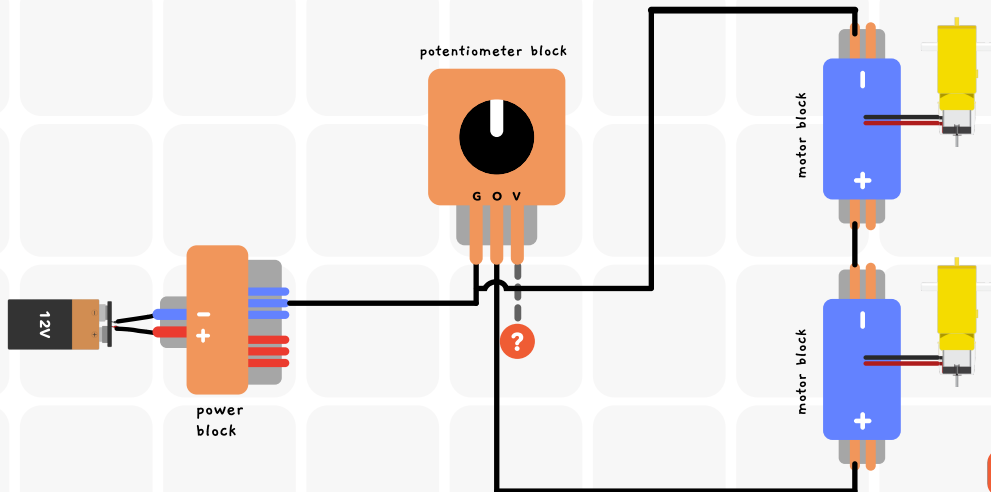


circuit 3 : potentiometer + switch block

Task: Use a potentiometer block to control the speed of 2 motor blocks connected in parallel. The circuit needs to be turned ON/OFF using a switch block. Can you complete missing wire **?** in the circuit and adjust the speed?

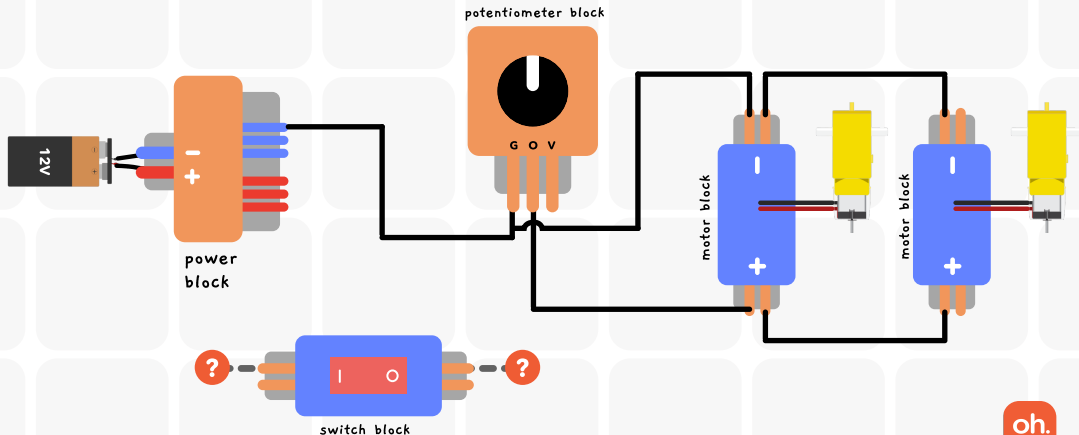

circuit 4 : parallel circuit

Task: Make a parallel circuit with the following and find the missing block  and missing wires  to complete the circuit.

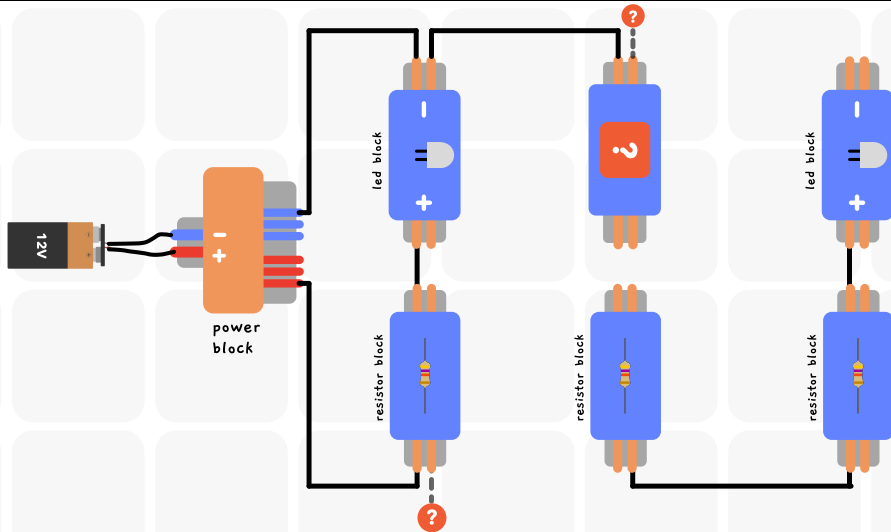

circuit 5 : series circuit

Task: Make a series circuit with the following and find the missing block ? and missing wire ? to complete the circuit.

